

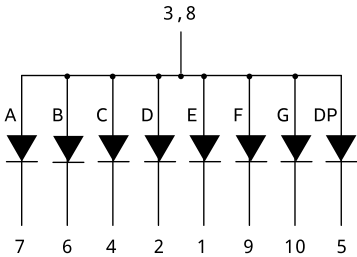


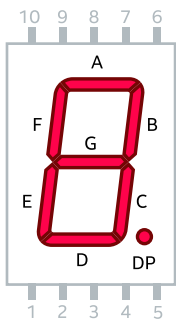

DOWNLOAD CODE
<https://github.com/GalileoWorkshop/IESC>

Seven-Segment Display Exercise

Seven Segment Display

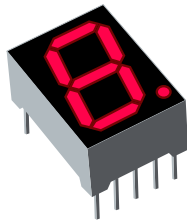

Build the Circuit

You will need the following components:

1. Galileo Development Board
2. Breadboard
3. Seven Segment Display
4. Two 330-ohm resistors
5. Nine male-to-male jumper wires

